

## Structural Verilog Modelling

The structural modelling style is the lowest level of abstraction obtained using logic gates.

In this we assemble several blocks of code and allow the introduction of hierarchy in a design.

The connections between components are specified within component instantiation statements. These statements specify an instance of a component occurring within another component or the circuit. Each component instantiation statement is labelled with an identifier.

The module body provides an internal view, it describes the behaviour or structure of the component.

2d]

Aim:-

To develop structural verilog model for an 8-bit Carry select Adder (CSA) using a 4-bit Ripple Carry Adder (RCA)

Software Tools Used:-


Xilinx Vivado 2019.1

Theory:-

Carry select Adder is a parallel adder which can add 2  $n$ -bit numbers at a time.

Generally a CSA consists of Ripple Carry Adders and Multiplexers as shown. The advantages of a CSA are: its efficiency over a CLA. The addition of 2 bits is carried out with the help of 2 adders considering both cases, when carry is 0 and when carry is 1. After the calculation is done, correct sum and the correct carry is selected with the help of a MUX.

Here we require 3 4-bit RCA's and 1 2:1 MUX.

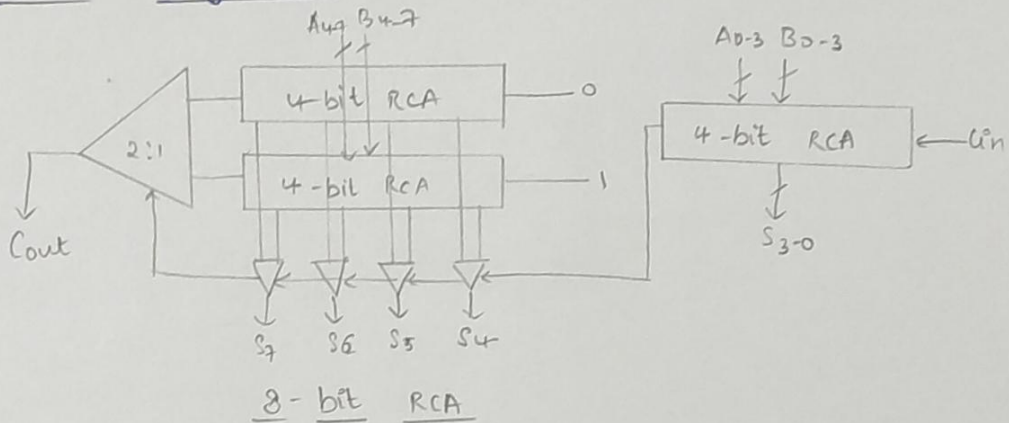Block Diagram:-Code + Testbench:-

```

module full_adder (a, b, cin, sum, carry);
  input  a, b, cin;
  output sum, carry;

```

```

  xor (sum, a, b, cin);
  and (w1, a, b);
  xor (w2, a, b);
  and (w3, w2, cin);
  or (carry, w3, w1);

```

```

endmodule

```

```

module RCA_4bit (A, B, CIN, SUM, CARRY);

```

```

  input  [3:0] A;

```

```

  input  [3:0] B;

```

```

  input  CIN;

```

```

  output [3:0] SUM;

```

```

  output CARRY;

```



```
wire w1, w2, w3;
```

```
full-adder FA1 (A[0], B[0], cin, sum[0], w1);
```

```
full-adder FA2 (A[1], B[1], w1, sum[1], w2);
```

```
full-adder FA3 (A[2], B[2], w2, sum[2], w3);
```

```
full-adder FA4 (A[3], B[3], w3, sum[3], carry);
```

```
endmodule
```

```
module Mux(a, b, sel, out);
```

```
input a, b;
```

```
input sel;
```

```
output out;
```

```
wire w1, w2;
```

```
and (w1, ~sel, a);
```

```
and (w2, sel, b);
```

```
or (out, w1, w2);
```

```
endmodule
```

```
module csa-8bit (a, b, cin, sum, cout);
```

```
input [7:0] a, b;
```

```
input cin;
```

```
output [7:0] sum;
```

```
output cout;
```

```
wire c;
```

```
wire [3:0] s1, s2;
```

```
wire c1, c2;
```

```
RCA_4bit rca_1 (.A(a[3:0]), .B(b[3:0]), .CIN(cin),
               .SUM(sum[3:0]), .CARRY(c));
```

```
RCA_4bit rca_2 (.A(a[7:4]), .B(b[7:4]), .CIN(1'b0),
               .SUM(s1[3:0]), .CARRY(c1));
```

```
RCA_4bit rca_3 (.A(a[7:4]), .B(b[7:4]), .CIN(1'b1),
               .SUM(s2[3:0]), .CARRY(c2));
```

```
MUX m1 (.a(s1[0]), .b(s2[0]), .sel(c), .out(sum[4]));
```

```
MUX m2 (.a(s1[1]), .b(s2[1]), .sel(c), .out(sum[5]));
```

```
MUX m3 (.a(s1[2]), .b(s2[2]), .sel(c), .out(sum[6]));
```



```
MUX m4 (.a(s1[3]), .b(s2[3]), .sel(c), .out(sum[7]));
```

```
MUX m5 (.a(c1), .b(c2), .sel(c), .out(cout));
```

```
endmodule
```
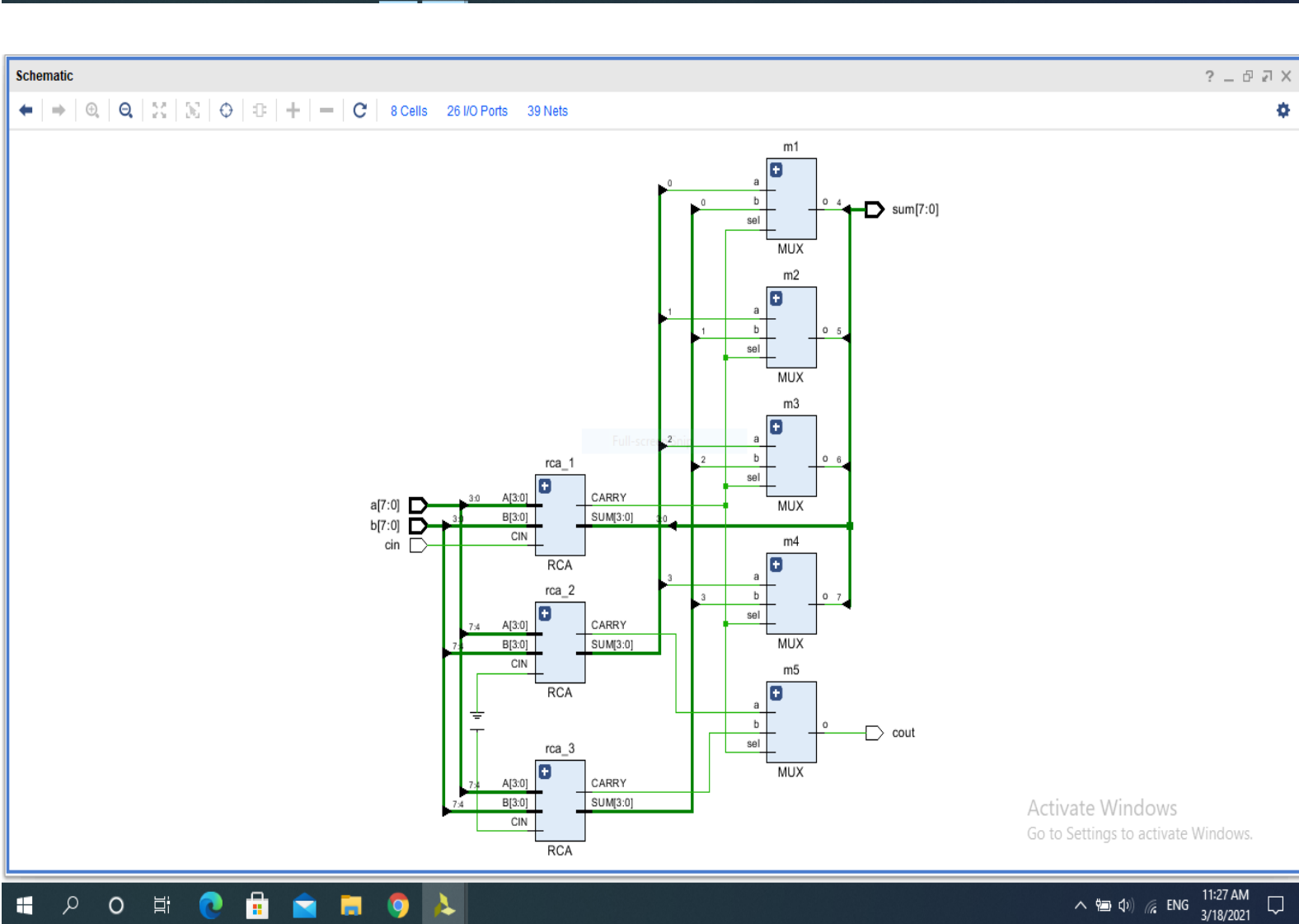 
### Result:-

We have instantiated and integrated lower level modules to design / attain higher-level functionality. We used RCA-Mux, to construct a Carry Select Adder (8 bits).





2c] Aim:-

To develop a structural verilog model for a 16-bit adder by cascading an 8-bit Kogge Stone Adder / Ripple Carry Adder.

Software / Tools Used:-

Xilinx Vivado 2019.1

Theory:-

Adder is one of the most commonly used digital feature in the sketch of a digital built-in circuit. Carry is an important part of an adder. To construct a 16-bit adder, we can cascade 2 - 8-bit adders. Here we cascade an 8-bit Kogge-Stone Adder to a Ripple Carry Adder (8 bit). The carry-out of the first stage will be the carry-in of the second stage. By cascading the modules using the basics of structural verilog and primitives, we are able to add two 16-bit numbers and obtain the sum and carry.

We can test the working of our verilog code by giving random 16-bit numbers in the testbench.

Code + Testbench:-

```

module KSA (A, B, S, Cin, Cout);
    input [7:0] A, B;
    input Cin;
    output [7:0] S;
    output Cout;
    wire [7:0] G1, P1, P2, G2, G3, P3, G4, P4, G5, P5, C;

    assign G1 = A & B;
    assign P1 = A ^ B;

    assign G2[0] = G1[0];
    assign P2[0] = P1[0];

    assign G2[1] = G1[1] | (P1[1] & G1[0]);
    assign P2[1] = P1[1] & P1[0];

    assign G2[2] = G1[2] | (P1[2] & G1[1]);
    assign P2[2] = P1[2] & P1[1];

    assign G2[3] = G1[3] | (P1[3] & G1[2]);
    assign P2[3] = P1[3] & P1[2];

    assign G2[4] = G1[4] | (P1[4] & G1[3]);
    assign P2[4] = P1[4] & P1[3];

    assign G2[5] = G1[5] | (P1[5] & G1[4]);
    assign P2[5] = P1[5] & P1[4];

    assign G2[6] = G1[6] | (P1[6] & G1[5]);
    assign P2[6] = P1[6] & P1[5];

```



assign  $G_2[7] = G_1[7] \mid (P_1[7] \& G_1[6]);$   
 assign  $P_2[7] = P_1[7] \& P_1[6];$

assign  $G_3[0] = G_2[0];$   
 assign  $P_3[0] = P_2[0];$

assign  $G_3[1] = G_2[1];$   
 assign  $P_3[1] = P_2[1];$

assign  $G_3[2] = G_2[2] \mid (P_2[2] \& G_2[0]);$   
 assign  $P_3[2] = P_2[2] \& P_2[0];$

assign  $G_3[3] = G_2[3] \mid (P_2[3] \& G_2[1]);$   
 assign  $P_3[3] = P_2[3] \& P_2[1];$

assign  $G_3[4] = G_2[4] \mid (P_2[4] \& G_2[2]);$   
 assign  $P_3[4] = P_2[4] \& P_2[2];$

assign  $G_3[5] = G_2[5] \mid (P_2[5] \& G_2[3]);$   
 assign  $P_3[5] = P_2[5] \& P_2[3];$

assign  $G_3[6] = G_2[6] \mid (P_2[6] \& G_2[4]);$   
 assign  $P_3[6] = P_2[6] \& P_2[4];$

assign  $G_3[7] = G_2[7] \mid (P_2[7] \& G_2[5]);$   
 assign  $P_3[7] = P_2[7] \& P_2[5];$

assign  $G_4[0] = G_3[0];$   
 assign  $P_4[0] = P_3[0];$

assign  $G_4[1] = G_3[1];$   
 assign  $P_4[1] = P_3[1];$

assign  $G_4[2] = G_3[2];$   
 assign  $P_4[2] = P_3[2];$

assign  $G4[3] = G3[3] | (P3[3] \& G3[6]);$   
 assign  $P4[3] = P3[3] \& P3[0];$   
  
 assign  $G4[4] = G3[4] | (P3[4] \& G3[1]);$   
 assign  $P4[4] = P3[4] \& P3[1];$   
  
 assign  $G4[5] = G3[5] | (P3[5] \& G3[2]);$   
 assign  $P4[5] = P3[5] \& P3[2];$   
  
 assign  $G4[6] = G3[6] | (P3[6] \& G3[3]);$   
 assign  $P4[6] = P3[6] \& P3[3];$   
  
 assign  $G4[7] = G3[7] | (P3[7] \& G3[4]);$   
 assign  $P4[7] = P3[7] \& P3[4];$   
  
 assign  $G5[0] = G4[0];$   
 assign  $P5[0] = P4[0];$   
  
 assign  $G5[1] = G4[1];$   
 assign  $P5[1] = P4[1];$   
  
 assign  $G5[2] = G4[2];$   
 assign  $P5[2] = P4[2];$   
  
 assign  $G5[3] = G5[3];$   
 assign  $P5[3] = P4[3];$   
  
 assign  $G5[4] = G4[4] | (P4[4] \& G3[0]);$   
 assign  $P5[4] = P4[4] \& P4[0];$   
  
 assign  $G5[5] = G4[5] | (P4[5] \& G3[1]);$   
 assign  $P5[5] = P4[5] \& P4[1];$   
  
 assign  $G5[6] = G4[6] | (P4[6] \& G3[2]);$   
 assign  $P5[6] = P4[6] \& P4[2];$



```

assign G5[7] = G4[7] | (P4[7] & G3[3]);
assign P5[7] = P4[7] & P4[3];

```

```

assign C = G5;
assign S[0] = P1[0] ^ Cin;
assign S[1] = P1[1] ^ C[0];
assign S[2] = P1[2] ^ C[1];
assign S[3] = P1[3] ^ C[2];
assign S[4] = P1[4] ^ C[3];
assign S[5] = P1[5] ^ C[4];
assign S[6] = P1[6] ^ C[5];
assign S[7] = P1[7] ^ C[6];
assign Cout = C[7];

```

```
endmodule
```

```
module KSA_tb();
```

```

reg [7:0] a, b;
reg C_in;
wire [7:0] sum;
wire c_out;

```

```

KSA dut (.A(a), .B(b), .Cin(C_in), .S(sum), .Cout
(c_out));

```

```
initial begin
```

```

a = 8'b10100101; b = 8'b1110100; C_in = 0;
end

```

```
endmodule
```



```
module RCA_8bit (A,B, cin, sum, CARRY);
```

```
input [7:0] A;
```

```
input [7:0] B;
```

```
input cin;
```

```
output [7:0] sum;
```

```
output CARRY;
```

```
wire w1;
```

```
RCA_4bit RCA1 (A[3:0], B[3:0], cin, sum[3:0], w1);
```

```
RCA_4bit RCA2 (A[7:4], B[7:4], w1, sum[7:4], CARRY);
```

```
endmodule
```

```
module cascade_16bit (a, b, cin, sum, cout);
```

```
input [15:0] a, b;
```

```
input cin;
```

```
output [15:0] sum;
```

```
output cout;
```

```
wire c;
```

```
RCA_8bit rca1 (.A (a[7:0]), .B (b[7:0]), .cin (cin),  
               .sum (sum[7:0]), .CARRY (c));
```

```
RCA_8bit rca2 (.A (a[15:8]), .B (b[15:8]), .cin (sum[15:8]),  
               .cin (c), .cout (cout));
```

```
endmodule
```

```

module cascade_16bit_tb();
reg [15:0] a,b;
reg cin;
wire [15:0] sum;
wire cout;

cascade_16bit dut (.a(a), .b(b), .cin(cin), .sum(sum),
                  .cout(cout));



initial begin
a = 16'b0000000000000000; b = 16'b0000000000000000;
cin = 0;
#10
a = 16'b1111111111111111; b = 16'b0010101010101010;
cin = 0;
#10
a = 16'b1111 001010100010; b = 16'b0100010111 01001;
cin = 1;
#10
a = 16'b0101010101010101; b = 16'b1010101010101010;
cin = 1;
#10
$stop;
end

endmodule

```
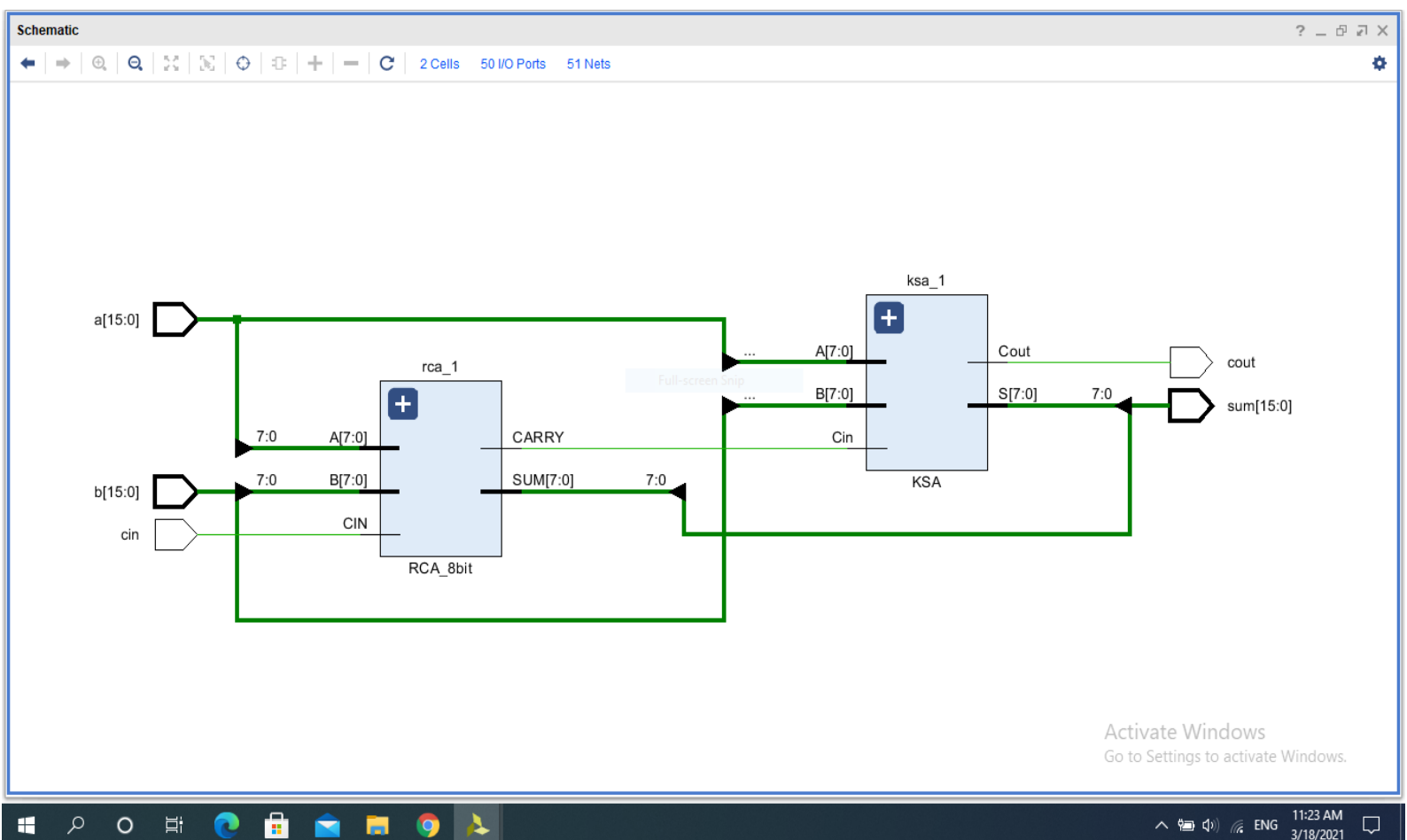 
### Result:-

Here we observe that instantiation of lower level modules for the construction of higher level module is indeed a powerful concept in HDL.





28) Aim:-

To develop a 4 bit up-down counter asynchronous verilog model.

Software Used:-


Xilinx Vivado 2019.1

Theory:-

By adding up the ideas of UP and DOWN counters, we can design an asynchronous up/down counter. It can count either ways, up to down or down to up, based on the clock signal input.

The up/down counter is slower than up counter or a down counter, because the addition propagation delay will get added to the NAND gate network.

Block Diagram:-

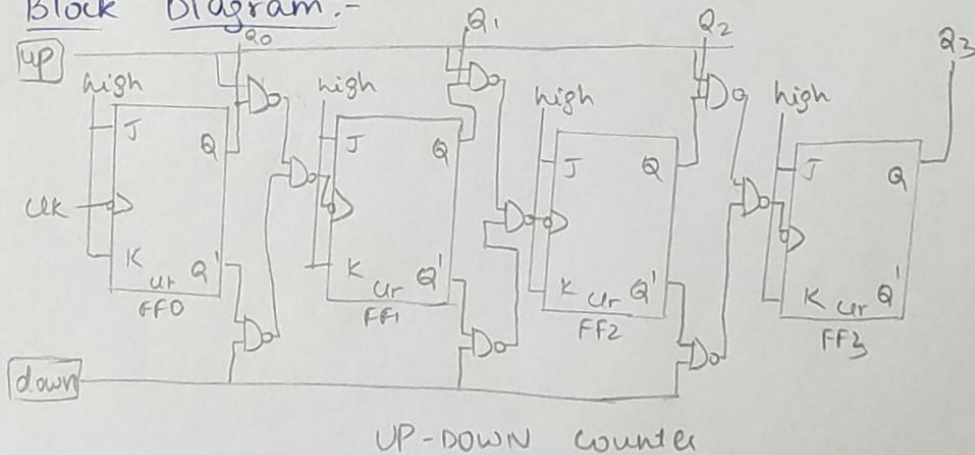

Code + Testbench:-

```

module counter_4bit (UD, clk, reset, Q)
input UD;
input clk;
input reset;
output [3:0] Q;
reg [3:0] Q = 4'b0000;

always @ (posedge clk or posedge reset)
if (reset == 1)
    Q <= 4'b0000;
else
    if (UD == 1)
        if (Q == 4'b1111)
            Q <= 4'b0000;
        else
            Q <= 4'b0001 + Q;
    else if (UD == 0)
        if (Q == 4'b0000)
            Q <= 4'b1111;
        else
            Q <= Q - 4'b0001;

end module

```

```

module counter_4bit_tb ();
reg ud, clk, rst;
wire [3:0] q;

```

```
counter_4bit dut(.UD(ud), .Q(q), .clk(clk),  
                .reset(rst));
```

```
initial
```

```
    clk = 1'b0;
```

```
always
```

```
    #5 clk = ~clk;
```

```
initial begin
```

```
    #0
```

```
    ud = 0; rst = 0;
```

```
    #20;
```

```
    ud = 1; rst = 0;
```

```
    #60;
```

```
    ud = 1; rst = 1;
```

```
end
```

```
endmodule
```

Result:-

We have written the Verilog code for a 4-bit up-down counter. To check if it is working fine, we wrote the testbench and observed the waveform.



